

Chapter-3 Logic gates



Modern VLSI Design 4e: Chapter 3

Copyright © 2008 Wayne Wolf

Gate design

Why designing gates for logic functions is non-trivial:

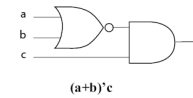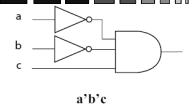- may not have logic gates in the library for all logic expressions;
- a logic expression may map into gates that consume a lot of area, delay, or power.



Two logic networks are equivalent but with different structures. Which is best depends on the requirements—the relative importance of area and delay—and the characteristics of the technology.

Modern VLSI Design 4e: Chapter 3

Copyright © 2008 Wayne Wolf

Gate design...

- We must work with both logic expressions and gate networks to find the best implementation of a function, *keeping in mind*:
- combinational logic expressions are the specification;
- logic gate networks are the implementation;
- area, delay, and power are the costs.

Modern VLSI Design 4e: Chapter 3

Copyright © 2008 Wayne Wolf

Completeness (*universality*)

- A set of functions $f1, f2, \dots$ is complete (universal) if every Boolean function can be generated by a combination of the functions.
- Complete (universal): NAND, NOR
- AND, OR are not complete.

If your set of logic gates is not complete, you can't design arbitrary logic.

Modern VLSI Design 4e: Chapter 3

Copyright © 2008 Wayne Wolf


Static complementary gates

One family of logic gate circuits: the *static complementary gate*


- *Complementary*: have complementary pullup (p-type) and pulldown (n-type) networks.
- *Static*: do not rely on stored charge.
- Simple, effective, reliable; hence ubiquitous.

Static complementary gate structure


Pullup and pulldown networks:

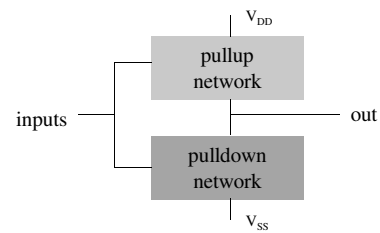


Inverter

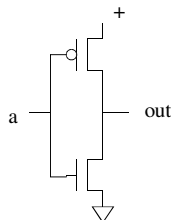

Inverter layout

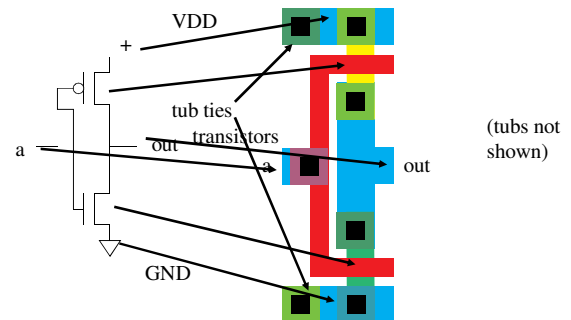


NAND gate

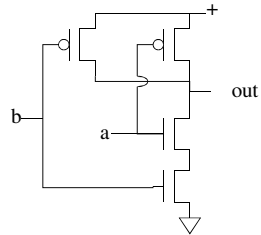

Modern VLSI Design 4e: Chapter 3

Copyright © 2008 Wayne Wolf


NAND layout

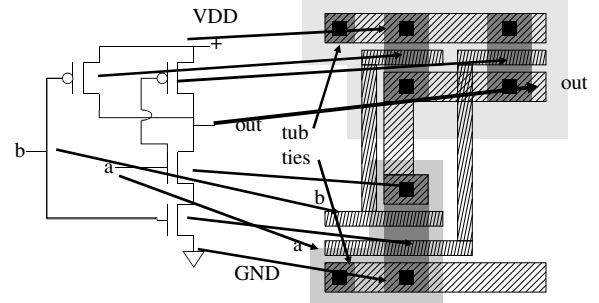

Modern VLSI Design 4e: Chapter 3

Copyright © 2008 Wayne Wolf


NOR gate

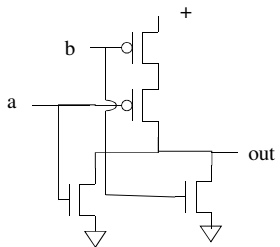

Modern VLSI Design 4e: Chapter 3

Copyright © 2008 Wayne Wolf

NOR layout

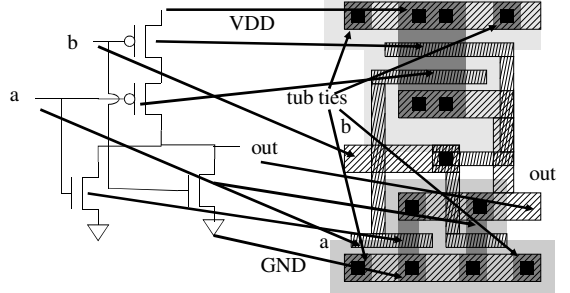

Modern VLSI Design 4e: Chapter 3

Copyright © 2008 Wayne Wolf

AOI/OAI gates



- AOI = and/or/invert; OAI = or/and/invert.
- Implement larger functions.
- Pullup and pulldown networks are compact: smaller area, higher speed than NAND/NOR network equivalents.
- AOI312: *AND* 3 inputs, *AND* 1 input (dummy), *OR* together these terms; then invert.

Modern VLSI Design 4e: Chapter 3

Copyright © 2008 Wayne Wolf

AOI example

$$\text{out} = [ab+c]':$$

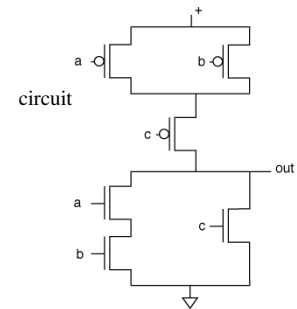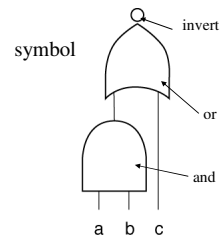

Modern VLSI Design 4e: Chapter 3

Copyright © 2008 Wayne Wolf

Pullup/pulldown network design

- Pullup and pulldown networks are duals.
- To design one gate, first design one network, then compute dual to get other network.
- Example: design network which pulls down when output should be 0, then find dual to get pullup network.

Modern VLSI Design 4e: Chapter 3

Copyright © 2008 Wayne Wolf

Quiz

- Design the static complementary pullup and pulldown networks for the $(a+b+c)'$ function
- Write the defining logic expression and transistor topology for AOI=22 complex gate.

Modern VLSI Design 4e: Chapter 3

Copyright © 2008 Wayne Wolf