 



Limitations of left-edge algorithm

- Some combinations of nets require more than one horizontal segment per net.



Dogleg wire

 - A dogleg wire has more than one horizontal segment.




Combinational network delay.

Sources of delay

- Gate delay:
 - drive;
 - load.
- Wire:
 - lumped load;
 - transmission line.


Fanout

- Fanout adds capacitance.

 


Ways to drive large fanout

 - Increase sizes of driver transistors. Must take into account rules for driving large loads.



Buffers

 Add intermediate buffers. This may require/allow restructuring of the logic.



Wire capacitance

- Use layers with lower capacitance.
- Redesign layout to reduce length of wires with excessive delay.

Placement and wire capacitance

